



**higher education  
& training**

Department:  
Higher Education and Training  
**REPUBLIC OF SOUTH AFRICA**

# **MARKING GUIDELINE**

**NATIONAL CERTIFICATE  
APRIL EXAMINATION  
INDUSTRIAL ELECTRONICS N1**

**5 APRIL 2016**

**This marking guideline consists of 6 pages.**

**QUESTION 1**

- 1.1
- |        |   |
|--------|---|
| 1.1.1  | I |
| 1.1.2  | M |
| 1.1.3  | B |
| 1.1.4  | C |
| 1.1.5  | J |
| 1.1.6  | D |
| 1.1.7  | K |
| 1.1.8  | G |
| 1.1.9  | H |
| 1.1.10 | A |
- (10 × 1) (10)
- 2.1
- 1.2.1
- $$I = \frac{P}{V_T}$$
- $$I = \frac{900 \times 10^{-3}}{1,5 + 1,5}$$
- $$I = 0,3A$$
- (3)
- 1.2.2
- $$R = \frac{V_T}{I}$$
- $$R = \frac{3}{0,3}$$
- $$R = 10\Omega$$
- (3)
- 1.3
- Readily available
  - Easy to install
  - Relatively cheap
  - Physically small
- (Any appropriate 4 × 1) (4)
- [20]**

**QUESTION 2**

- 2.1
- Outside the magnet they move from the north pole to the south pole.
  - Inside the magnet they move from the south pole to the north pole.
  - They are continuous and form a complete path.
  - They never intersect so they never cross one another.
  - They are parallel to one another.
  - They are invisible and pass through all materials.
  - They always enter or leave a magnetic material at right angles.
  - They tend to be elastic.
- (Any 4 × 1) (4)

## INDUSTRIAL ELECTRONICS N1

$$\begin{aligned}
 2.2 \quad 2.2.1 \quad R_{TOTALS} &= R_1 + R_2 + R_3 \\
 R_{TOTAL} &= 200 + 400 + 600 \\
 R_{TOTAL} &= 1200\Omega \qquad (3)
 \end{aligned}$$

$$\begin{aligned}
 2.2.2 \quad I_T &= \frac{V_T}{R_T} \\
 I_T &= \frac{36}{1200} \\
 I_T &= 0,03A \qquad (3)
 \end{aligned}$$

$$\begin{aligned}
 2.2.3 \quad V_{R1} &= I_T \times R_1 \\
 V_{R1} &= 0,03 \times 200 \\
 V_{R1} &= 6V \qquad (3)
 \end{aligned}$$

$$\begin{aligned}
 2.2.4 \quad P &= I^2 \times R_T & \text{OR} & \quad P = V_T \times I_T & \text{OR} & \quad P = \frac{V^2}{R} \\
 P &= 0,03^2 \times 1200 & & \quad P = 36 \times 0,03 & & \quad P = \frac{36^2}{1200} \\
 P &= 1,08W & & \quad P = 1,08W & & \quad P = 1,08W \qquad (4)
 \end{aligned}$$

- 2.3
- Yellow
  - Violet
  - Orange
- (3)  
**[20]**

**QUESTION 3**

$$\begin{aligned}
 3.1 \quad R &= \frac{\rho L}{A} \\
 R &= \frac{1,728 \times 10^{-6} \times 70}{4 \times 10^{-6}} \\
 R &= 30,24\Omega \qquad (3)
 \end{aligned}$$

$$\begin{aligned}
 3.2 \quad R_T &= R_O(1 + \alpha_O t) \\
 R_T &= 11(1 + 0,0042 \times 33) \\
 R_T &= 12,52\Omega \qquad (3)
 \end{aligned}$$

INDUSTRIAL ELECTRONICS N1





3.3	3.3.1	$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$ $\frac{1}{C_T} = \frac{1}{1,8} + \frac{1}{2,1} + \frac{1}{1,0}$ $\frac{1}{C_T} = \frac{21+18+3,78}{37,8}$ $\frac{1}{C_T} = \frac{42,78}{37,8}$ $\frac{C_T}{1} = \frac{37,8}{42,78}$ $C_T = 0,88\mu F$	OR	$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$ $\frac{1}{C_T} = \frac{1}{1,8} + \frac{1}{2,1} + \frac{1}{1,0}$ $\frac{1}{C_T} = 0,56 + 0,476 + 0,1$ $\frac{1}{C_T} = 1,136$ $\frac{C_T}{1} = \frac{1}{1,136}$ $C_T = 0,88\mu F$	(4)
-----	-------	---	----	--	-----

3.3.2	$Q = C \times V$ $Q = 0,88 \times 10^{-6} \times 100$ $Q = 88\mu F$	(3)
-------	---	-----

3.4.1	$V_S = \frac{V_P \times N_S}{N_P}$ $V_S = \frac{220 \times 1}{10}$ $V_S = 22V$	(4)
-------	--	-----


3.4.2	$I_S = \frac{I_P \times N_P}{N_S}$ $I_S = \frac{2 \times 10}{1}$ $I_S = 20A$	(3) <b>[20]</b>
-------	--	--------------------

**QUESTION 4**

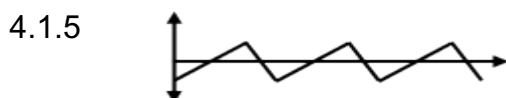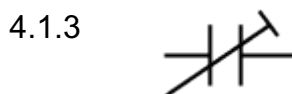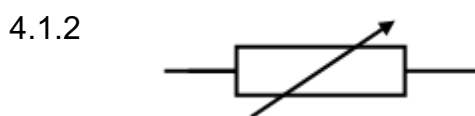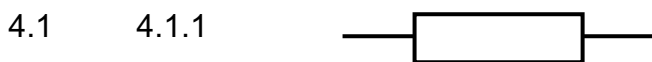


INDUSTRIAL ELECTRONICS N1

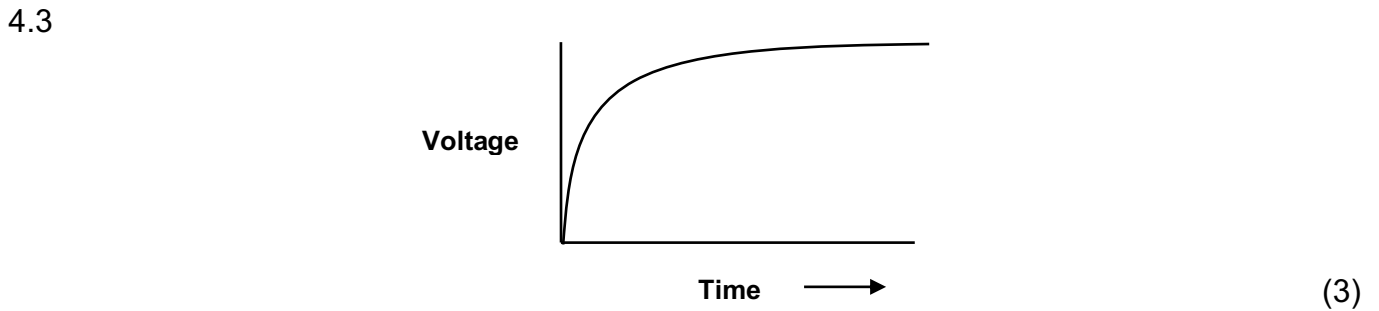4.2 It is the number of cycles completed in one second. (3)



4.4 When one cell is drained it acts as a load for the other cells as well, causing them to drain even faster. (2)

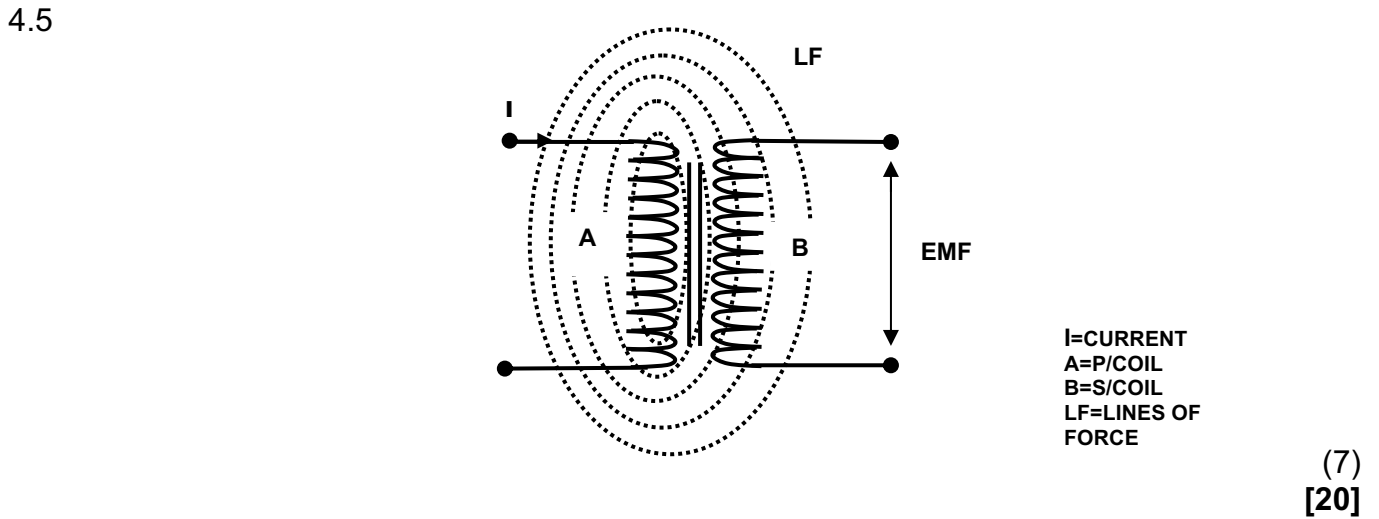

**QUESTION 5**

- 5.1.1 False
- 5.1.2 False
- 5.1.3 False
- 5.1.4 True
- 5.1.5 True
- 5.1.6 True
- 5.1.7 False
- 5.1.8 False
- 5.1.9 False
- 5.1.10 True

(10 × 1) (10)

5.2	<ul style="list-style-type: none"><li>• Protons</li><li>• Neutrons</li></ul>		(2)
5.3.1	Centre-tap transformer		(2)
5.3.2	<ul style="list-style-type: none"><li>• There is no negative cycle on the output waveform.</li><li>• D2 is responsible for the faulty condition.</li></ul>	(2 × 2)	(4)
5.3.3	D2 is not conducting		(2)
			<b>[20]</b>
		<b>TOTAL:</b>	<b>100</b>