



# higher education & training

---

Department:  
Higher Education and Training  
**REPUBLIC OF SOUTH AFRICA**

T690(E)(A5)T  
**APRIL EXAMINATION**

**NATIONAL CERTIFICATE**

**INDUSTRIAL ELECTRONICS N1**

(8080641)

**5 April 2016 (X-Paper)**  
**09:00–12:00**

**This question paper consists of 6 pages and 1 formula sheet.**

**DEPARTMENT OF HIGHER EDUCATION AND TRAINING**  
**REPUBLIC OF SOUTH AFRICA**  
NATIONAL CERTIFICATE  
INDUSTRIAL ELECTRONICS N1  
TIME: 3 HOURS  
MARKS: 100

---

**INSTRUCTIONS AND INFORMATION**

1. Answer ALL the questions.
  2. Read ALL the questions carefully.
  3. Number the answers according to the numbering system used in this question paper.
  4. Write neatly and legibly.
-

**QUESTION 1**

- 1.1 Choose an item from COLUMN B that matches a description in COLUMN A. Write only the letter (A–M) next to the question number (1.1.1–1.1.10) in the ANSWER BOOK.

COLUMN A		COLUMN B	
1.1.1	Provide larger currents	A	coil
1.1.2	Is available in various sizes	B	electrons
1.1.3	Flow from negative terminal to positive terminal	C	capacitor
1.1.4	Stores a charge	D	transistor
1.1.5	Capacitor value increases	E	magnetic
1.1.6	Has a collector as a terminal	F	dielectric
1.1.7	Core of a transformer	G	transformer
1.1.8	Mutual induction	H	wire wound resistor
1.1.9	Gives a very accurate value	I	secondary cells
1.1.10	An inductor	J	parallel connection
		K	shell
		L	series connection
		M	primary cell

(10 × 1) (10)

- 1.2 A cellular telephone uses two 1,5 volt cells in series as a power source and consumes 900 milliwatt.

Calculate the following:

- 1.2.1 Current flow at 900 milliwatt  
1.2.2 Minimum resistance of the cellular telephone

(2 × 3) (6)

- 1.3 Give FOUR advantages of primary cells

(4)  
**[20]**

**QUESTION 2**

- 2.1 State FOUR characteristics of the magnetic lines of force. (4)
- 2.2 Three resistors with values of 200 ohm, 400 ohm and 600 ohm are connected in series across a 36 volt direct current power source.
- Calculate the following:
- 2.2.1 Total resistance of the circuit (3)
- 2.2.2 Total current flow through the circuit (3)
- 2.2.3 Voltage drop through the 200 ohm resistor (3)
- 2.2.4 Power consumed in the circuit (4)
- 2.3 Give the colour code for the  $4k7\Omega$  resistor (3)

**[20]****QUESTION 3**

- 3.1 A copper conductor is 70m long and has a cross-sectional area of  $4 \text{ mm}^2$ . The resistivity of copper is  $1,728 \times 10^{-6} \Omega\text{m}$ .
- Calculate the resistance of the conductor. (3)
- 3.2 A tube filled with Mercury has a resistance of  $11 \Omega$  at  $0^\circ\text{C}$ . The temperature coefficient of Mercury is  $0,0042 \Omega/^\circ\text{C}$ .
- If the tube is heated to  $33^\circ\text{C}$  what will be its resistance? (3)
- 3.3 Three capacitors with values of  $1,8 \mu\text{F}$ ,  $2,1 \mu\text{F}$  and  $10 \mu\text{F}$  respectively are connected in series.
- Calculate the following:
- 3.3.1 Total capacitance of the circuit (4)
- 3.3.2 Charge across the circuit with an applied voltage of 100 V (3)
- 3.4 A transformer has an input voltage of 220 V and a turns ratio of 10 : 1. The primary current is 2 A.
- Calculate the following:
- 3.4.1 Secondary voltage (4)
- 3.4.2 Current flow through the secondary (3)

**[20]**

**QUESTION 4**


- 4.1 Sketch the IEC symbol for the following components:
- 4.1.1 Fixed resistor
  - 4.1.2 Variable resistor
  - 4.1.3 Pre-set capacitor
  - 4.1.4 Inductor
  - 4.1.5 Saw-tooth waveform
- (5 × 1) (5)
- 4.2 Define the term *frequency of the waveform*. (3)
- 4.3 Make a sketch to show a charging curve for a capacitor in terms of voltage and time. (3)
- 4.4 Give ONE disadvantage of connecting cells in parallel. (2)
- 4.5 Mutual induction occurs when two coils are placed next to one another.  
Make a neat, labelled sketch to show mutual induction between two coils. (7)
- [20]**

**QUESTION 5**

- 5.1 Indicate whether the following statements are TRUE or FALSE. Choose the answer and write only 'true' or 'false' next to the question number (5.1.1–5.1.10) in the ANSWER BOOK.
- 5.1.1 The polarity of a neutron is positive.
  - 5.1.2 An insulator has an abundance of free electrons.
  - 5.1.3 A cation is formed when electrons are added to an atom.
  - 5.1.4 A pentavalent atom is a donor atom.
  - 5.1.5 The process where arsenic is added to germanium is called donor doping.
  - 5.1.6 Pentavalent atoms have five valency electrons.
  - 5.1.7 Trivalent atoms have six valency electrons.
  - 5.1.8 When a trivalent atom is added to silicon it will create an abundance of electrons.
  - 5.1.9 A transistor is a semiconductor rectifier device.
  - 5.1.10 A transistor can be likened to two diodes connected back-to-back.
- (10 × 1) (10)

5.2 Name TWO particles of a nucleus of an atom. (2)

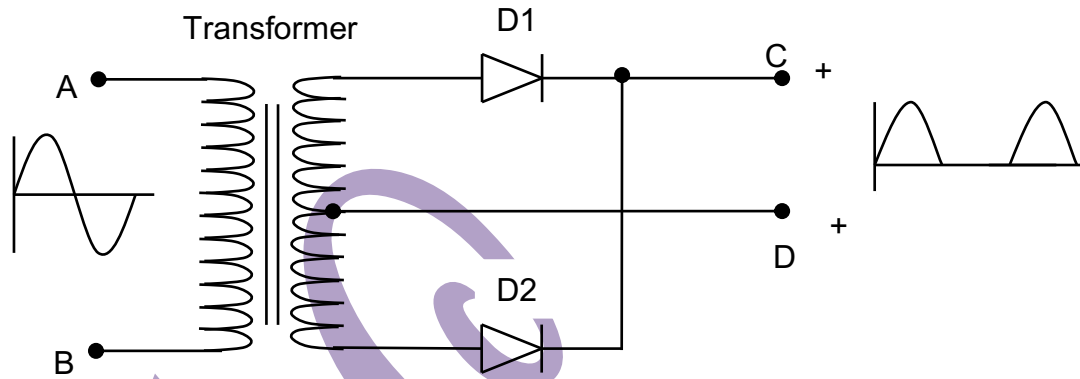5.3 Refer to the FIGURE below that shows the circuit diagram of a full-wave rectifier with two diodes and answer the questions.



**FIGURE**

5.3.1 Give the name of the transformer that is used. (2)

5.3.2 The output wave form at C and D shows a faulty condition.  
Name the faulty condition and the component that has caused the faulty condition. (2 × 2) (4)

5.3.3 What could be the problem with the faulty component mentioned in QUESTION 5.3.2? (2)

**[20]**

**TOTAL: 100**

**INDUSTRIAL ELECTRONICS N1****FORMULA SHEET**

$$I = \frac{V}{R}$$

$$I = \frac{E}{R + r}$$

$$P = V \times I$$

$$R_t = R_1 + R_2 + \dots + R_n$$

$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

$$C_t = C_1 + C_2 + \dots + C_n$$

$$\frac{1}{C_t} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$

$$Q = C \times V$$

$$L_t = L_1 + L_2 + \dots + L_n$$

$$\frac{1}{L_t} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$$

$$\frac{V_p}{V_s} = \frac{N_p}{N_s} = \frac{I_s}{I_p}$$

$$R_t = R_o(1 + \alpha_o t)$$

$$R = \frac{\rho \ell}{A}$$